

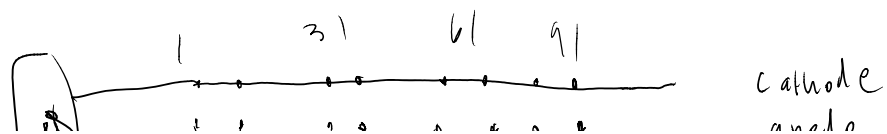
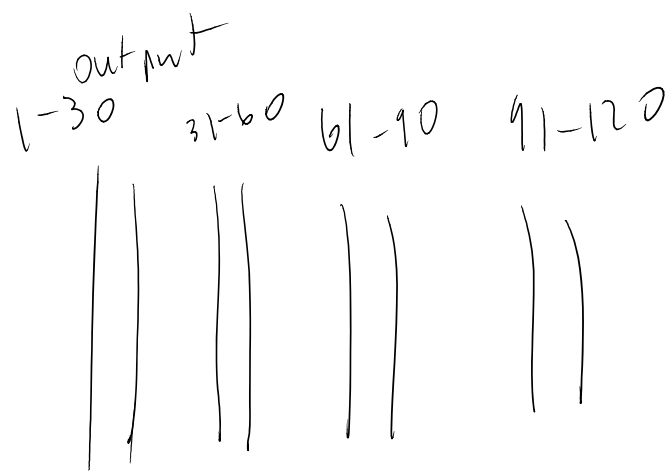
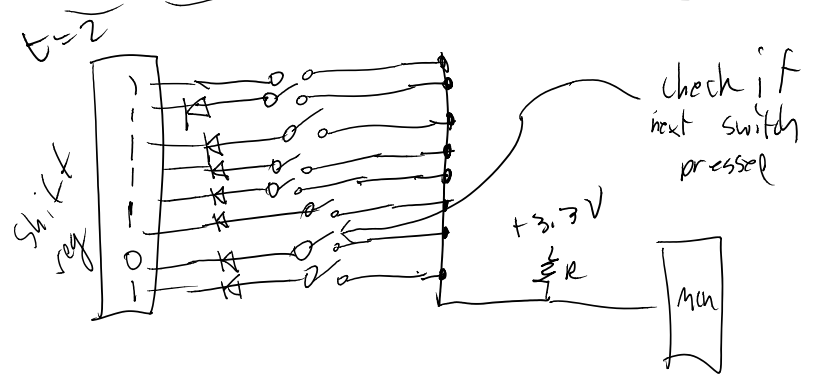
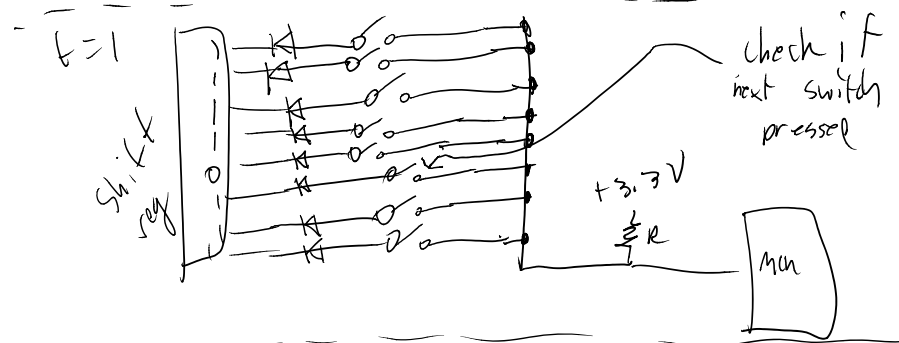
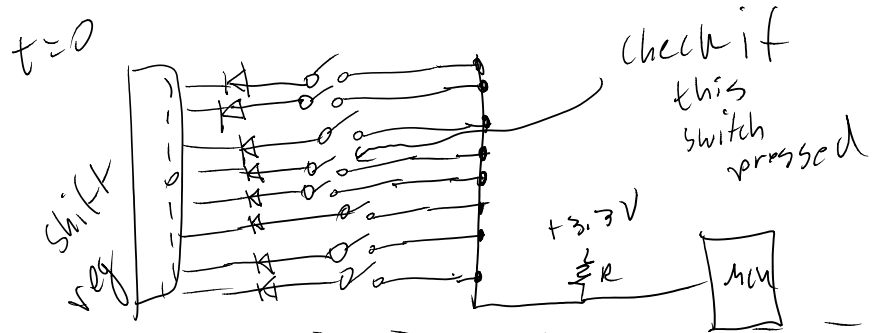


# Digital Cribbage Board Design

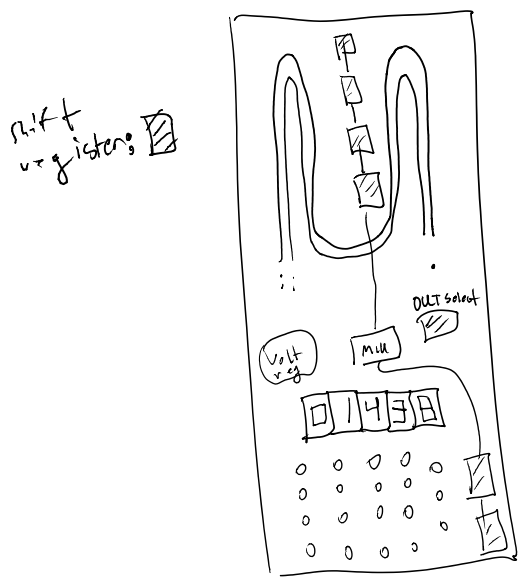

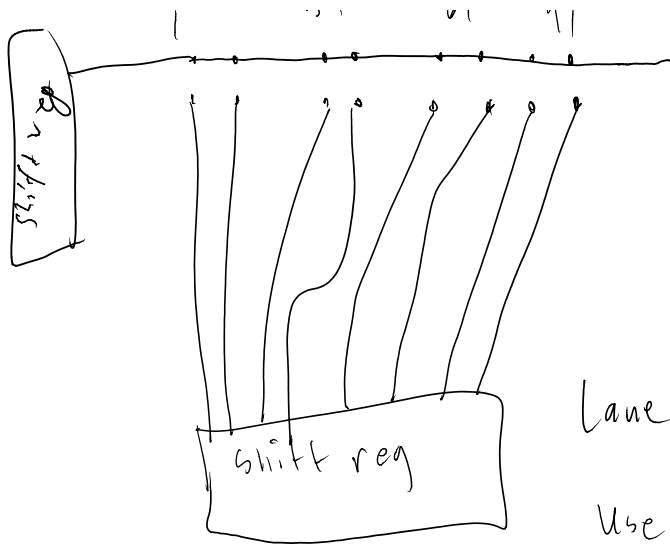

cathode  
anode

lane/player select

Use multiplexing to cycle  
through 8 of them